

---

# Design Guidelines for RT7302 and RT7304 PSR LED Driver

## Abstract

[RT7302](#) and [RT7304](#) are constant current LED drivers with active power factor correction (PFC). They support high power factor across a wide range of line voltages, and drive the converter in the quasi-resonant (QR) mode to achieve higher efficiency. By using primary side regulation (PSR), [RT7302/RT7304](#) control the output current accurately without the need of a shunt regulator or opto-coupler at the secondary side, reducing the external component count, the cost, and the size of the driver board.

This application note presents a step by step design guideline for an isolated single stage constant current LED driver with PFC using the [RT7302](#). The guideline can also be applied to [RT7304](#).

The design example in this application note describes an 18W LED driver with slim form-factor, suitable for T8 LED tube applications, but the same design can also be used in LED bulb or other form factor applications.

## Contents

1. Introduction.....	2
2. RT7302 Basic Operation.....	3
3. Design of an 18W LED Driver for T8 Applications.....	5
4. Design Tool Explanation.....	13
5. Circuit Diagram of the Evaluation Board.....	15
6. Electrical Performance Measurements.....	18
7. PCB Layout Information.....	21
8. Summary.....	22

## 1. Introduction

[RT7302](#) and [RT7304](#) are constant current LED drivers with active power factor correction (PFC). They support high power factor across a wide range of line voltages, and drive the converter in the quasi-resonant (QR) mode to achieve higher efficiency. By using primary side regulation (PSR), [RT7302/RT7304](#) control the output current accurately without a shunt regulator or opto-coupler at the secondary side, reducing the external component count, the cost, and the size of the LED driver board.

[RT7304](#) embeds comprehensive protection functions for robust designs, including LED open circuit protection, LED short circuit protection, output diode short circuit protection, VDD under voltage lockout (UVLO), VDD over-voltage protection (VDD OVP), over-temperature protection (OTP), and cycle-by-cycle current limitation. [RT7304](#) is available in a cost effective SOT-23-6 package.

[RT7302](#) has the same basic functionality as [RT7304](#), but integrates more features, including fast startup via high voltage pin, PWM dimming, and input voltage feed-forward compensation. [RT7302](#) is available with SOP-8 package.

This application note presents a step by step design guideline for an isolated single stage constant current LED driver with PFC using the [RT7302](#). The design guideline can also be applied to [RT7304](#).

The design example in this application note is an 18W LED driver with slim form-factor, suitable for T8 LED tube applications.

 


Figure 1. Picture of the 18W evaluation board with a typical T8 LED assembly

## 2. RT7302 Basic Operation

Figure 2 shows [RT7302](#) in a typical flyback converter topology with input voltage ( $V_{in}$ ).

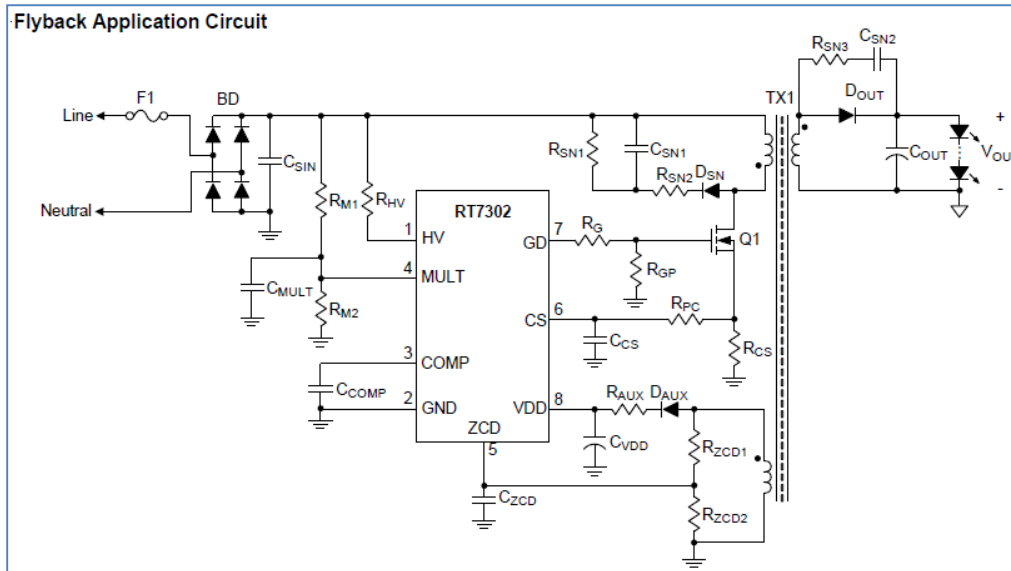


Figure 2

When main switch Q1 is turned on with a fixed on-time  $t_{on}$ , the peak current  $I_{L\_pk}$  of the magnetic inductor  $L_m$  can be calculated by the following equation:

$$I_{L\_pk} = \frac{V_{in}}{L_m} \times t_{on}$$

If the input voltage is the output voltage of the full-bridge rectifier with sinusoidal input voltage  $V_{in\_pk} \cdot \sin(\theta)$ , the inductor peak current  $I_{L\_pk}$  can be expressed as the following equation:

$$I_{L\_pk} = \frac{V_{in\_pk} |\sin(\theta)| \times t_{on}}{L_m}$$

When the converter operates in critical-conduction mode (CRM) with constant on-time control, the envelope of the peak inductor current will follow the input voltage waveform in-phase. Thus, high power factor can be achieved. The minimum on time is set by the upper divider resistor of the ZCD network  $R_{ZCD1}$ .

Quasi resonant switching is achieved by sensing the auxiliary winding zero current condition and a smart internal valley detection circuit. Switch-on of the MOSFET will always happen at a valley of the resonant voltage, thereby reducing switching losses and EMI. The ZCD pin is also used to sense output OVP condition, set by  $R_{ZCD2}$ .

The primary peak current is sensed by measuring the voltage across the MOSFET source resistor via the CS pin. An internal leading edge blanking circuit removes any spikes from this signal. A current variation due to a propagation delay is compensated by the CS pin internal current source and the external series resistor  $R_{PC}$ .

The MULT pin is used for sensing the input peak voltage, and controls the ramp for T-on generation. The line voltage sense is used as feed-forward to adjust the ramp for constant COMP voltage over line voltage. This improves the regulation, eases compensation and achieves accurate maximum power limit over the full mains range. This is especially important for full range LED driver designs.

[RT7302](#) HV pin will quickly charge the capacitor connected to the VDD pin during start-up. After start-up, the HV pin is disconnected, and the VDD is supplied by the auxiliary winding. This method ensures fast start-up without extra power dissipation in the bleeder resistor during normal operation.

**Design Procedure:**

The basic design sequence is as following:

Define Input and output conditions → Calculate input power → Transformer design, Calculate N ratio, Primary inductance, Primary and secondary winding turns → Current sense resistor ( $R_{CS}$ ), bridge rectifier, MOSFET parameters, Output diode parameters → Minimum ton setting ( $R_{ZCD1}$ ) → OVP setting ( $R_{ZCD2}$ ) → Propagation delay setting ( $R_{PC}$ ) → Feed-forward compensation ( $R_{M1}$ ,  $R_{M2}$ )

The [RT7302 design tool](#) can be used to quickly determine the component values. Chapter 3 contains a detailed step by step design description for the 18W reference design.

### 3. Design of an 18W LED Driver for T8 Applications

The LED driver example for this section is the 18W T8 LED driver evaluation board, see Figure 3.



Figure 3. The board measures 230x18x10mm and will fit in most narrow tube T8 housing behind the LED board.

Requirement specification for this design:

- Input range: 90V ~ 264V<sub>ac</sub>
- LED load: 45V / 400mA
- Efficiency >85% at 120V / 230V<sub>ac</sub>
- PF: > 0.95 and THDi < 15% (meet IEC61000-3-2 class C & D)

#### Step 1. Input and Output Conditions

The input and output conditions are listed as follows:

maximum AC input voltage  $V_{ac\_max}$ , 264V<sub>ac</sub>

minimum AC input voltage  $V_{ac\_min}$ , 90V<sub>ac</sub>

line frequency  $f_{line}$ , 50Hz / 60Hz

average output current  $I_o$ , 400mA

minimum average output voltage  $V_{o\_min}$ , 43V

maximum average output voltage  $V_{o\_max}$ , 47V

LED string is using 14 high power LEDs with total dynamic resistance of 14Ω

Estimated maximum average input power  $P_{in\_max\_est}$  can be expressed as:

$$P_{in\_max\_est} = \frac{V_{o\_max} \cdot I_o}{\eta} \quad \text{where } \eta \text{ is the estimated efficiency.}$$

The efficiency is estimated at 85%, the input power will become :  $47 \cdot 0.4 / 0.85 = 22.12W$ .

Estimated peak current transfer ratio of the transformer ( $CTR_{TX1}$ ) can be expressed as

$$CTR_{TX1} = \frac{I_{SEC\_PK}}{I_{PRI\_PK}} \times \frac{N_s}{N_p}$$

where  $I_{SEC\_pk}$  is the peak current of secondary side,  $I_{PRI\_pk}$  is the peak current of the primary side,  $N_S$  is the turn's number of the secondary winding, and  $N_P$  is the turn's number of the primary winding.  $CTR_{TX1}$  can be estimated to be 0.9.

The reflected output voltage  $V_{ro}$  can be express as

$$V_{ro} = \frac{N_P}{N_S} \cdot (V_{O\_max} + V_f)$$

where  $V_f$  is the forward voltage of output diode.  $V_{ro}$  is recommended to be within 95 ~125V.

In the example: Set  $V_{ro} = 125V$ .

Min. VDD supply voltage at max. output voltage  $V_{DD\_Vomax\_min}$  can be derived as

$$V_{DD\_Vomax\_min} = \frac{V_{O\_max}}{V_{O\_min}} \cdot V_{TH\_OFF\_max} \cdot 130\%$$

where  $V_{TH\_OFF}$  is the falling under voltage lockout (UVLO) threshold voltage of the controller.

VDD supply voltage at max. output voltage  $V_{DD\_max}$  must be within  $V_{DD\_Vomax\_min} \sim V_{DD\_OVP\_min}$ .

In the example:

$V_{O\_max} = 47V$ ,  $V_{O\_min} = 43V$ ,  $V_{TH\_OFF\_max} = 10V$ ,  $V_{DD\_Vomax\_min} = 14.2V$

Set  $V_{DD\_max} = 20V$ .

Output Capacitor  $C_{OUT}$  Calculation:

The output capacitor value will determine the amount of voltage ripple on the LED string. This voltage ripple, together with the dynamic resistance of the LED string will determine the current ripple through the LED string and this will cause 100Hz or 120Hz light flicker.

In this example the maximum allowed LED current ripple amplitude is set at 340mA<sub>pp</sub> for a ripple percentage of 42%. The LED string uses 14 LEDs and has total dynamic resistance of 14Ω:  $V_{OUT\_ripple} = 0.34A \cdot 14\Omega = 4.76V_{pp}$ . The transformer secondary winding current can estimated having a low frequency ripple of double the line frequency and low frequency peak to peak amplitude of double the average output current. The output capacitor value can now be calculated:

$$C_{OUT} = \frac{I_{OUT\_PP}}{V_{OUT\_PP} \cdot 2 \cdot \pi \cdot f}$$

where  $I_{OUT\_PP}$  is 2x the average LED current, and  $V_{OUT\_PP}$  is the allowed AC output voltage ripple and  $f$  is double line frequency. Calculating for 50Hz line frequency:  $C_{OUT} = 2 \cdot 0.4 / (4.76 \cdot 2 \cdot \pi \cdot 100) = 267 \mu F$ . For less LED current ripple, the  $C_{OUT}$  value needs to be increased. But when LED strings with higher dynamic resistance are used, the  $C_{OUT}$  value can be reduced.

## Step 2. Transformer Design

Ideal turn's ratio of primary to secondary windings can be expressed as

$$\frac{N_P}{N_S} = \frac{V_{ro}}{V_{o\_max} + V_f}$$

In the example:

$$V_{ro} = 125V, V_{o\_max} = 47V, V_f = 0.7V, N_P/N_S = 2.62$$

Ideal turn's ratio of secondary to auxiliary windings can be expressed as

$$\frac{N_S}{N_A} = \frac{V_{o\_max}}{V_{DD\_max}}$$

In the example:

$$V_{o\_max} = 47V, V_{DD\_max} = 20V, N_S/N_A = 2.35$$

The maximum on time of the MOSFET  $t_{on\_max}$  can be expressed

$$t_{on\_max} = D_{on\_max} \cdot \frac{1}{f_{s\_min}}$$

in which  $f_{s\_min}$  is the minimum switching frequency.

The duty ratio of the MOSFET  $D_{on}$  can be expressed

$$D_{on\_max} = \frac{V_{ro}}{V_{ro} + V_{ac\_min\_pk}}$$

The primary-side inductance  $L_m$  can be derived as

$$L_m = \frac{t_{on}}{2I_o} \cdot \frac{N_P}{N_S} \cdot CTR_{TX1} \frac{\int_0^{\frac{1}{2f_{line}}} \frac{V_{ac}(t)^2}{V_{ro} + V_{ac}(t)} dt}{\frac{1}{2f_{line}}}$$

Thus,  $L_m$  can be obtained after the minimum switching frequency  $f_{s\_min}$  is determined.

In the example:

Set  $f_{s\_min} = 54\text{kHz}$ ,

$V_{ro} = 125\text{V}$ ,  $V_{ac\_min\_pk} = 127\text{V}$ ,

Obtain  $t_{on\_max} = 8.68\mu\text{s}$  and  $L_m = 899\mu\text{H}$

The minimum number of turns for the transformer primary side to avoid the core saturation is given by:

$$N_{P\_min} > \frac{I_{P\_pk} \cdot L_m}{B_{max} \cdot A_e}$$

where  $A_e$  is the cross-sectional area of the core in  $\text{m}^2$ , and  $B_{max}$  is the maximum flux density in Gauss.

In the example:

$I_{P\_pk} = 1.23\text{A}$ ,  $L_m = 899\mu\text{H}$ , EDR-28 core is chosen and its  $A_e = 88\text{m}^2$ .

Set  $B_{max} = 2950$  Gauss. Obtain  $N_{P\_min} > 42.5$  turns.

Now all the parameters of transformer are determined, including  $N_{P\_min}$ ,  $N_P/N_S$ ,  $N_S/N_A$  and  $L_m$ .

$N_P = 43\text{T}$ ,  $N_S = 43/2.62 = 16.4\text{T}$ , choose 16T,  $N_A = 16/2.35 = 6.8\text{T}$ , choose 7T.

### Step 3. Current Sense Resistor Determination

Current sense resistor  $R_{CS}$  can be determined as the following equation:

$$R_{CS} = \frac{1}{2} \times \frac{N_P}{N_S} \times \frac{K_{CC}}{I_O} \times CTR_{TX1}$$

where  $K_{CC}$  is a reference in the controller.

In the example:

Actual  $N_P/N_S = 2.69$ ,  $K_{CC} = 0.25$ ,  $I_O = 0.4\text{A}$ ,  $CTR_{TX1} = 0.9$ ,

The current sense resistor  $R_{CS}$  will become  $(1/2) \times 2.69 \times (0.25/0.4) \times 0.9 = 0.79 \Omega$ .

### Step 4. Bridge Rectifier Determination

The maximum reverse voltage of the bridge rectifier  $V_{RRM\_max}$  can be expressed as:

$$V_{RRM\_max} = \sqrt{2} \cdot V_{ac\_max}$$

The maximum forward current of the bridge rectifier  $I_{BR\_max}$  can be expressed as:



$$I_{BR\_max} = \frac{P_{in\_max}}{V_{ac\_min}}$$

In the example:

$$V_{RRM\_max} = \sqrt{2} \cdot 264 = 373V$$

$$I_{BR\_max} = 22.12/90 = 0.25A$$

A 600V / 1A diode bridge will provide sufficient de-rating, including inrush current and voltage surge.

## Step 5. MOSFET Determination

The maximum drain-to-source voltage stress of the MOSFET  $V_{DS\_max}$  is given as:

$$V_{DS\_max} = V_{RRM\_max} + V_{clamp}$$

in which  $V_{clamp}$  is the maximum voltage on the snubber and it must be higher than  $V_{ro}$ .

The maximum drain-to-source current stress of the MOSFET  $I_{DS\_max}$  is given as:

$$I_{DS\_max} = \sqrt{2} \cdot V_{ac\_min} \cdot \frac{t_{on\_max}}{L_m}$$

In the example:

$$\text{Set } V_{clamp} = 160V$$

$$V_{DS\_max} = 373+160 = 533V : \text{ for sufficient de-rating, choose at least 650V rated MOSFET.}$$

$I_{DS\_max} = I_{P\_pk} = 1.23A$  : MOSFET  $R_{dson}$  selection depends on thermal aspects. In this small T8 design, a 4A MOSFET with  $R_{dson}$  of  $1.8\Omega$  was selected, which can be used without heat-sink.

## Step 6. Output Diode and Auxiliary Diode Determination

The maximum reverse voltage stress of the output diode  $V_{Do\_max}$  can be expressed as:

$$V_{Do\_max} = V_{RRM\_max} \cdot \frac{N_s}{N_p} + V_{O\_OVP}$$

where  $V_{O\_OVP}$  is the output over voltage level.

The maximum average forward current stress of the output diode  $I_{Do\_max}$  can be expressed as:

$$I_{Do\_max} = I_o$$

In the example:

$$\text{Set } V_{O\_OVP} = 61V$$

$$V_{Do\_max} = 373/2.62 + 61 = 203V$$

$$I_{Do\_max} = I_o = 0.4A$$

Diodes with higher current rating can be chosen for higher efficiency.

The maximum reverse voltage stress of the auxiliary diode  $V_{Da\_max}$  can be expressed as:

$$V_{Da\_max} = V_{RRM\_max} \cdot \frac{N_A}{N_P} + V_{DD\_OVP}$$

where  $V_{DD\_OVP}$  is the VDD over voltage level.

The maximum average forward current stress of the output diode  $I_{Da\_max}$  can be expressed as:

$$I_{Da\_max} = I_{DD\_max}$$

in which  $I_{DD\_max}$  is the maximum supply current for the controller.

In the example:

$$V_{DD\_OVP} = 27V$$

$$V_{Da\_max} = 373/(2.62 * 2.35) + 27 = 87.8V$$

$$I_{Da\_max} = I_{DD\_max} = 5mA$$

### Step 7. Minimum On-Time Setting

[RT7302](#) limits a minimum on-time  $t_{on\_min}$  for each switching cycle. The  $t_{on\_min}$  is a function of the sample-and-hold ZCD current  $I_{ZCD\_SH}$  as following:

$$t_{on\_min} \cdot I_{ZCD\_SH} = 405 \text{ p} \cdot \text{sec} \cdot A \text{ (typ.)}$$

$I_{ZCD\_SH}$  can be expressed as:

$$I_{ZCD\_SH} = \frac{V_{in} \cdot N_A}{R_{ZCD1} \cdot N_P}$$

Thus,  $R_{ZCD1}$  can be determined by:

$$R_{ZCD1} = \frac{t_{on\_min} \cdot V_{in}}{405p} \cdot \frac{N_A}{N_P} \text{ (typ.)}$$

In addition, the current flowing out of ZCD pin must be lower than 2.5mA (typ.). Thus, the  $R_{ZCD1}$  is also determined by:

$$R_{ZCD1} > \frac{\sqrt{2} \cdot V_{ac\_max}}{2.5m} \cdot \frac{N_A}{N_P}$$

In the example:

$$R_{ZCD1} > \sqrt{2} * 264 / 2.5mA / (2.62 * 2.35) = 24.2k\Omega$$

Set  $R_{ZCD1} = 60k\Omega$

When  $V_{in} = 10V$ ,  $t_{on\_min} = 405p * 60k * (2.62 * 2.35) / 10 = 14.9\mu s$

In general, longer  $t_{on\_min}$  can slightly improve THDi. However, if  $t_{on\_min}$  is too long, it will induce a current resonance at  $V_{in}$  zero crossing, worsening THDi. Thus,  $t_{on\_min}$  can be properly defined according to the measured THDi.

## Step 8. Output Over-Voltage Protection Setting

Output OVP is achieved by sensing the knee voltage on the auxiliary winding. Thus,  $R_{ZCD1}$  and  $R_{ZCD2}$  can be determined by the equation as:

$$V_{O\_OVP} \cdot \frac{N_A}{N_S} \cdot \frac{R_{ZCD2}}{R_{ZCD1} + R_{ZCD2}} = 3.1V \text{ (typ.)}$$

In the example:

Set  $V_{O\_OVP} = 61V$

It can be calculated that  $R_{ZCD2} = 7.9k\Omega$

## Step 9. Propagation Delay Compensation Design

The  $V_{CS}$  deviation ( $\Delta V_{CS}$ ) caused by propagation delay effect can be derived as:

$$\Delta V_{CS} = \frac{V_{in} \cdot t_d \cdot R_{CS}}{L_m},$$

in which  $t_d$  is the delay period which includes the propagation delay of [RT7302](#) and the turn-off transition of the main MOSFET.

The sourcing current from CS pin of [RT7302](#)  $I_{CS}$  can be expressed as:

$$I_{CS} = K_{PC} \cdot V_{in} \cdot \frac{N_A}{N_P} \cdot \frac{1}{R_{ZCD1}}$$

where  $K_{PC}$  is a constant value in the controller.  $R_{PC}$  can be designed by:

$$R_{PC} = \frac{\Delta V_{CS}}{I_{CS}}$$

$$= \frac{t_d \cdot R_{CS} \cdot R_{ZCD1}}{L_m \cdot K_{PC}} \cdot \frac{N_P}{N_A}$$

$t_d$  is estimated to be around 150ns

In the example:

$$R_{PC} = 150n \cdot 0.74 \cdot 60k / (899\mu \cdot 0.02) \cdot (2.62 \cdot 2.35) = 2.3k\Omega$$

The delay period  $t_d$  is varied with the parasitic capacitance of MOSFET, the gate driving capability, and the propagation delay of the controller. Thus,  $t_d$  cannot be estimated accurately, and  $R_{PC}$  may need to be modified according to the measured output current. If the output current increases when  $V_{in}$  rises,  $R_{PC}$  should be increased. If the output current decreases with  $V_{in}$  rises,  $R_{PC}$  should be decreased.

### Step 10. Feed-Forward Compensation Design (Only for [RT7302](#))

The COMP voltage,  $V_{COMP}$ , can be derived from the following equations.

$$\frac{1}{2} (V_{MULT\_pk})^2 \times \frac{t_{on} + t_{off}}{t_s} \times G_{m_{ramp}} \times t_{on} = C_{ramp} \times V_{COMP}$$

$$V_{MULT\_pk} = V_{in\_pk} \times \frac{R_{M2}}{R_{M1} + R_{M2}}$$

$V_{MULT\_pk}$  is the peak voltage on the MULT pin.  $G_{m_{ramp}}$  is the trans-conductance of the ramp generator, and its typical value is  $2.5\mu A/V$ .  $C_{ramp}$  is the capacitance of the ramp generator, and its typical value is 6.5pF. When the converter operates at CRM,  $(t_{on} + t_{off}) / t_s = 1$ .  $V_{COMP\_min}$  is recommended to be within 1.2 ~ 1.5V, and  $R_{M2}$  is recommended to be within 30 ~ 60k $\Omega$ . Thus, the voltage divider resistors  $R_{M1}$  and  $R_{M2}$  can be determined according to the above parameters.

In the example:

$t_{on\_max} = 8.68\mu s$ .

Set  $V_{COMP\_min} = 1.2V$ ,

Obtain  $V_{MULT\_pk} = 0.85V$ .

Set  $R_{M2} = 43k\Omega$ ,

It can be calculated that  $R_{M1} = 6.4M\Omega$ .

## 4. Design Tool Explanation

The [RT7302 design tool](#) and [RT7304 design tool](#) can be used as quick way to determine the component values. The content is similar to the step by step design as described in Chapter 3. In the design tool, users input operation parameters into "Yellow Grid". According to the key-in parameter, the design tool will automatically generate the results in Pink Grid".

Table 1 below shows the entered data and calculation results for the 18W T8 reference design.

Table 1. Design tool data

Step1: Input and output conditions Definition		
Min. AC input voltage $V_{ac\_min}$	90	Vrms
Max. AC input voltage $V_{ac\_max}$	264	Vrms
Line frequency $f_{line}$	50	Hz
Average output current $I_o$	0.4	A
Min. average output voltage $V_{o\_min}$	43.0	V
Max. average output voltage $V_{o\_max}$	47.0	V
Max. average output power $P_{o\_max}$	18.8	W
Estimated efficiency $\eta$	85	%
Estimated peak current transfer ratio (CTR) of the transformer(TX <sub>1</sub> )	90	%
$(I_{sec\_pk} / I_{pri\_pk}) * (N_s / N_p) =$		
Estimated half of the resonant period of the primary-side inductance $L_m$ and parasitic capacitance of MOSFET $Q_1$	1.00	$\mu$ s
Estimated deviation of the detected inductance discharge time $T_{off}$	0.50	$\mu$ s
Estimated max. average input power $P_{in\_max\_est}$	22.12	W
Forward voltage of output diode $V_f$	0.7	V
Max. voltage of " $V_{o\_max} * N_p / N_s =$ " $V_{r0}$	125	V
Min. VDD supply voltage at $V_{o\_max}$ $V_{DD\_Vomax\_min}$	14.2	V
VDD supply voltage at $V_{o\_max}$ $V_{DD\_max}$	20	V
Step2: Transformer (TX <sub>1</sub> ) Design		
1. Turns ratio determination		
Ideal turns ratio of primary to secondary windings $N_p / N_s =$	2.62	
Ideal turns ratio of secondary to auxiliary windings $N_s / N_A =$	2.35	
2. Inductance design		
The lowest switching frequency $f_{s\_min}$	54.00	kHz
Max. on time of the MOSFET $t_{on\_max}$	8.68	$\mu$ s
Duty ratio at the peak of the min. AC input voltage $D_{on\_max}$	0.47	
Factor(t) at the min. AC input voltage Factor(t) <sub>min</sub>	35.13	
Primary-side Inductance $L_p =$	898.87	$\mu$ H
3. Current Stress Calculation (@min. AC input voltage and full load)		
Max. peak current of the primary winding $I_{p\_pk}$	1.229	A
RMS current of the primary winding $I_{p\_rms}$	0.369	A
Max. peak current of the secondary winding $I_{s\_pk}$	3.303	A
RMS current of the secondary winding $I_{s\_rms}$	0.912	A
4. Structure design		
Max. magnetic flux density $B_{max}$	2950	Gauss
Cross sectional area of core $A_c$	88	mm <sup>2</sup>
Min. turns number of the primary winding $N_{p\_min} >$	42.56	Turns
Turns number of the primary winding $N_p =$	43	Turns
Turns number of the secondary winding $N_s =$	16	Turns
Turns number of the auxiliary winding $N_A =$	7	Turns
Actual $N_p / N_s =$	2.69	
Actual $N_s / N_A =$	2.29	
Current Density $J =$	8	A/mm <sup>2</sup>
Wire Diameter of the Primary Winding $r_p \geq$	0.24	mm
Selected Wire Diameter of the Primary Winding $r_p =$	0.27	mm
Current density of the primary winding $J_{pri} =$	6.452	A/mm <sup>2</sup>
Total wire Area of Primary Winding $A_p =$	2.46	mm <sup>2</sup>
Wire Diameter of the Secondary Winding $r_s \geq$	0.38	mm
Selected Wire Diameter of the Secondary Winding $r_s =$	0.3	mm
Current density of the secondary winding $J_{sec} =$	12.908	A/mm <sup>2</sup>
Total wire Area of the Secondary Winding $A_s =$	3.14	mm <sup>2</sup>
Selected Wire Diameter of the Auxiliary Winding $r_A =$	0.12	mm
Total Wire Area of the Auxiliary Winding $A_A =$	0.08	mm <sup>2</sup>
Selected Transformer $A_w =$	23.10	mm <sup>2</sup>
Transformer Fill Factor $K_w =$	0.246	
Step3: Current Sense Resistor(R <sub>CS</sub> ) Determination		
Ideal current sense resistor $R_{CS} =$	0.79	$\Omega$
Selected current sense resistor $R_{CS} =$	0.74	$\Omega$
Actual average output current $I_o =$	0.429	A
Max. CS peak voltage $V_{CS\_pk\_max}$	0.91	V
Ratio of the $V_{CS\_CL}$ to $V_{CS\_pk\_max}$ $V_{CS\_CL} / V_{CS\_pk\_max} =$	1.02	
Step4: Bridge Rectifier(BD) Determination		
Max. reverse voltage of the bridge rectifier $V_{RRM\_max}$	373	V
Max. forward current of the bridge rectifier $I_{BR\_max}$	0.25	A
Step5: MOSFET(Q <sub>1</sub> ) Determination		
Max. voltage on the snubber $V_{clamp} =$	160.00	V
Max. D-to-S voltage stress of the MOSFET $V_{DS\_max}$	533.4	V
Max. D-to-S current stress of the MOSFET $I_{DS\_max}$	1.229	A
Step6: Output diode(D <sub>OUT</sub> ) and Auxiliary Diode(D <sub>AUX</sub> ) Determination		
Max. reverse voltage stress of the output diode $V_{DO\_max}$	200.0	V
Max. average forward current stress of the output diode $I_{DO\_max}$	0.400	A
Max. reverse voltage stress of the auxiliary diode $V_{DA\_max}$	87.8	V
Max. average forward current stress of the auxiliary diode $I_{DA\_max}$	5.000	mA
Step7: Min. on Time Design		
High-side resistor of the ZCD resistor-divider $R_{ZCD1} >$	24.31	k $\Omega$
$R_{ZCD1} =$	60.00	k $\Omega$
Min. on time @ $V_{CSIN} = 10V$ $t_{on(min)}$	14.93	$\mu$ s
Step8: OVP Setting		
Ratio of the output OV to max. output voltages $V_{o\_ovp} / V_{o\_max} =$	1.30	
Output over-voltage threshold $V_{o\_ovp}$	61.10	V
Low-side resistor of the ZCD resistor-divider $R_{ZCD2} =$	7.87	k $\Omega$
Step9: Propagation Delay Compensation Design		
IC Propagation delay+MOSFET turn off transition $t_D =$	150.00	ns
Propagation delay compensation resistor $R_{PC} =$	2.28	k $\Omega$
Step10: Feed-Forward Compensation Design		
Recommended Min. COMP voltage $V_{COMP\_min} =$	1.20	V
Recommended Min. MULT voltage $V_{MULT\_min} =$	0.85	V
Low-side resistor of the MULT resistor-divider $R_{M2} =$	43	k $\Omega$
High-side resistor of the MULT resistor-divider $R_{M1} =$	6.4	M $\Omega$
Step11: Recommended Component Value		
High-voltage start-up resistor $R_{HV} =$	10 ~ 22	k $\Omega$
External GATE-to-GND resistor $R_{gp} =$	10 ~ 22	k $\Omega$
Gate resistor between GATE pin and MOSFET(Q <sub>1</sub> ) gate $R_g =$	10 ~ 100	$\Omega$
Resistor in series with the diode(D <sub>AUX</sub> ) $R_{aux} =$	10 ~ 100	$\Omega$
Parallel resistor of the MOSFET snubber $R_{SH1} =$	100 ~ 300	k $\Omega$
Series resistor of the MOSFET snubber $R_{SH2} =$	100 ~ 300	$\Omega$
VDD decoupling capacitor $C_{VDD} =$	10 ~ 33	$\mu$ F
Compensation capacitor between the COMP and GND pins $C_{comp} =$	1 ~ 4.7	$\mu$ F
Filter capacitor between the MULT and GND pins $C_{MULT} =$	10 ~ 1000	pF (Dim)
Filter capacitor between the ZCD and GND pins $C_{ZCD} =$	1 ~ 100	nF (Nor)
Capacitor of the MOSFET snubber $C_{SH1} =$	10 ~ 22	pF
Capacitor of the MOSFET snubber $C_{SH2} =$	1 ~ 2.2	nF

## 5. Circuit Diagram of the Evaluation Board

The circuit diagram of the evaluation board is shown in Figure 4 below.

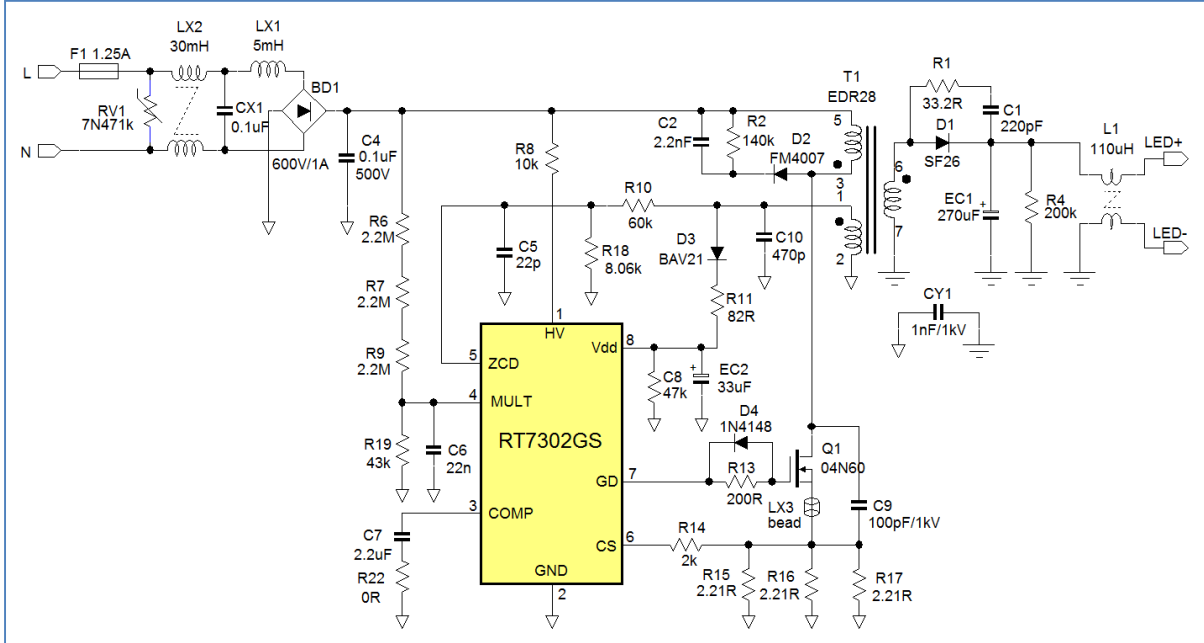


Figure 4. Schematic of the 18W T8 LED driver reference design

RV1 is added for line surge protection. LX2, CX1 and LX1 are added to reduce Line conducted EMI. L1 and LX3 are added to reduce radiated EMI.

The full BOM is shown in table 2 below.

Table 2. Full BOM of the 18W LED driver reference design

Item	Quantity	Reference	Part/Value	Type	Vendor	Remark
1	1	F1	T1.25A/300V	SS-5F-2P	Littlefuse	
2	1	RV1	7N471K	TVS-2P	Thinking	
3	1	LX2	30mH	LRS-T14	Abliss	T12.7*7.92*4.9(μ=10000)
4	1	CX1	0.1μF	CFS-12X12	Shiny Space	
5	1	LX1	5mH	LDS-D9X12	Mag. layers	
6	1	BD1	1A/600V	DB-1A	GW	
7	1	C4	0.1μF/500V	CFS-11X10	Murata	
8	3	R6, R7, R9	2.2MΩ	0805	RALEC	
9	1	R19	43kΩ	0603	RALEC	
10	1	C6	22nF/50V	0603	Murata	
11	1	C7	2.2μF/25V	0805	Murata	


12	1	R22	0Ω	0603	RALEC	
13	1	R8	10kΩ	1206	RALEC	
14	1	R2	140kΩ	1206	RALEC	
15	1	D2	FM4007	SOD123	Willas	
16	1	C2	2.2nF/1kV	1206	Murata	
17	1	R13	200Ω	0805	RALEC	
18	1	D4	1N4148	SOD-123	Willas	
19	1	Q1	4A/650V	TO-220	IPS	FTA04N65D
20	1	C9	100pF/1kV	1206	Murata	
21	1	LX3	T3.5*3*1.4	---	King core	On Source pin of Q1
22	3	R15, R16, R17	2.21Ω	1206	RALEC	
23	1	R14	2kΩ	603	RALEC	
24	1	C10	470pF/1kV	1206	Murata	
25	1	CY1	1000pF/250Vac	CAP-10mm	Murata	
26	1	R10	60kΩ	0603	RALEC	
27	1	R18	8.06kΩ	0603	RALEC	
28	1	C5	22pF	0603	Murata	
29	1	D3	BAV21	SOD-123	Willas	
30	1	R11	82Ω	0603	RALEC	
31	1	EC2	33μF/50V	CES-5X11	Rubycon	
32	1	T1	EDR28	EDR28	Abliss	
33	1	U1	<a href="#">RT7302</a>	SOP-8	Richtek	
34	1	D1	SF26	DO-15	Willas	
35	1	R1	33Ω	1206	RALEC	
36	1	C1	220pF/1kV	1206	Murata	
37	1	EC1	270μF/63V	CES-10X25	Rubycon	
38	1	L1	110μH	LR-T9	Abliss	T9*5*3(μi=10000)
39	1	R4	200kΩ	1206	RALEC	




**Transformer design:** The transformer design specification is shown in Figure 5.

Transformer Specification

Core Size:	EDR-28
Material:	PC40
Bobbin/PINs:	Horizontal / 7pins
Primary inductor: ( $\pm 5\%$ )	920 $\mu$ H
Leakage inductor:	30 $\mu$ H

 

Electrical:

 

Winding Specifications:

Winding No.	PIN	Wire	Turns	Winding Type	Tape Layer
N1	3 → 4	0.27φ	28Ts	Close winding	2 Layers
N2	6 → 7	Triple wire 0.3φ	16Ts	Close winding	2 Layers
N3	1 → 2	0.12φ x 4 parallel	7Ts	Close winding	1 Layer
N4	4 → 5	0.27φ	15T	Close winding	1 Layer

Figure 5. Transformer specification

The primary side formed by sandwich structure is used to reduce the leakage inductance of the transformer, improving the efficiency and the output current regulation. To improve radiation EMI, the maximum voltage swing which is on pin 3 of the transformer, should be at the most inner side. To meet the safety standard, Triple wire at the secondary side is normally adopted for providing insulation.

## 6. Electrical Performance Measurements

Table 3 below shows the LED driver input and output parameters over the full mains voltage range.

Table 3. Performance measurements

Frequency	Vac [V]	Pin [Watt]	Vout [V]	Iout [mA]	Pout [Watt]	Eff. [%]	PF Value	THD
60Hz	90	21.54	45.75	405	18.53	86.02%	0.9960	6.37
60Hz	100	21.24	45.78	405	18.54	87.29%	0.9960	6.68
60Hz	110	21.03	45.80	404	18.50	87.98%	0.9954	7.03
60Hz	120	20.87	45.83	403	18.47	88.50%	0.9950	7.24
60Hz	132	20.73	45.86	402	18.44	88.93%	0.9944	7.53
50Hz	180	20.60	46.00	401	18.45	89.54%	0.9908	7.51
50Hz	200	20.60	46.07	400	18.43	89.46%	0.9886	7.02
50Hz	220	20.64	46.15	400	18.46	89.44%	0.9851	6.73
50Hz	230	20.69	46.23	400	18.49	89.38%	0.9832	6.82
50Hz	240	20.75	46.31	400	18.52	89.27%	0.9811	6.99
50Hz	264	20.90	46.44	400	18.58	88.88%	0.9738	7.86

Current regulation = 1.23%

$\Delta$ Efficiency = 3.52%


Maximum PF = 0.996

Minimum PF = 0.974


As can be seen, the current line regulation is excellent. Driver efficiency meets the target easily, and Power Factor and THDi are fully in line with regulations for lighting applications.

The figures in Table 4 show voltage and current waveforms during various operation conditions:


Table 4. Measured waveforms during various operation conditions

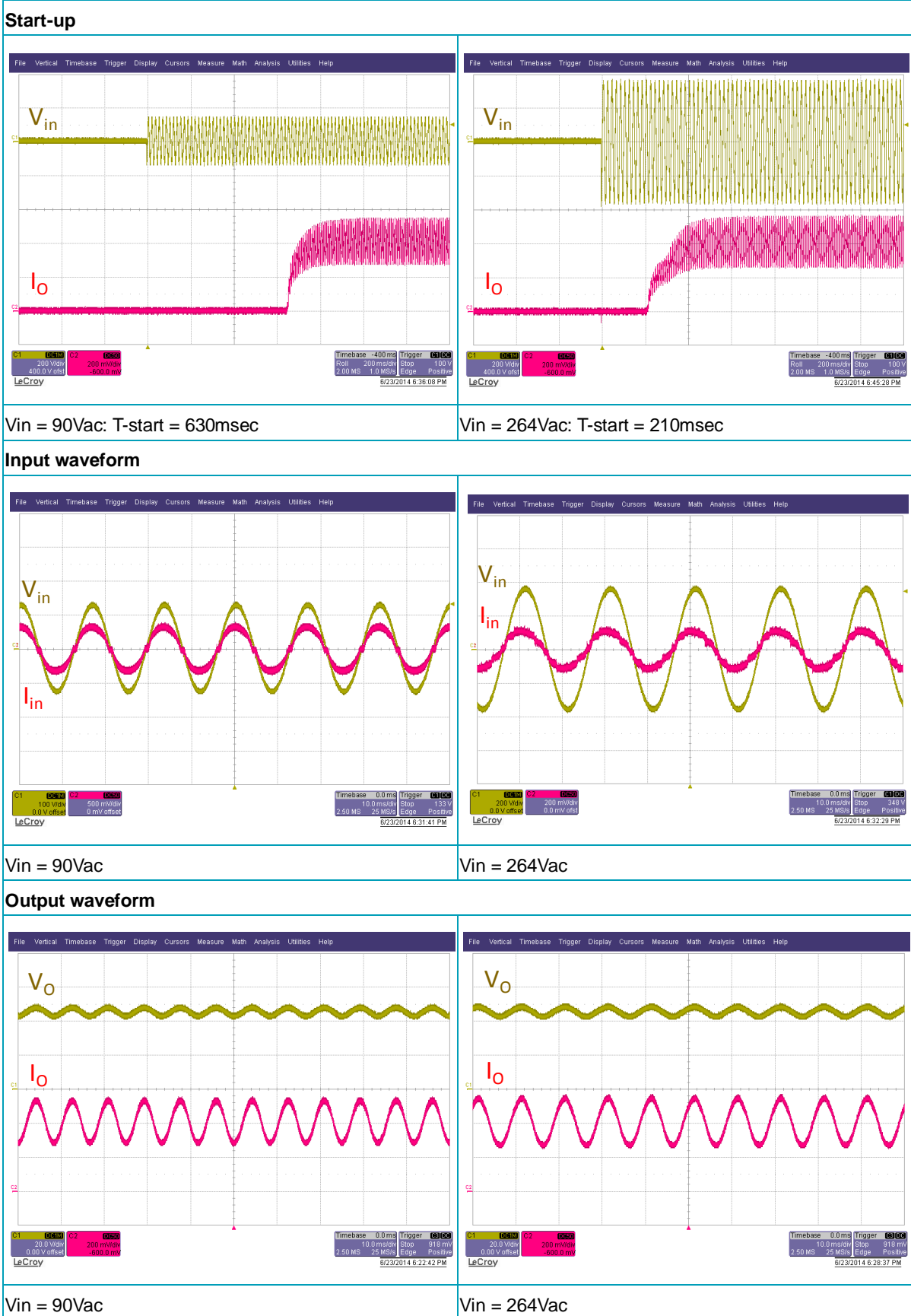

 **Harmonic content of input current: (IEC61000-3-2)**




Vin = 110Vac: passes Class C and D

 


Vin = 230Vac: passes Class C and D

**Conduction EMI**

 

Vin = 230V-L

 


Vin = 230V-N

The demo board passes conducted and radiated EMI at 120V and 230Vac
 
### 7. PCB Layout Information

The PCB layout of the reference design is shown in Figure 6 below. It is build from double-sided FR-4 material and uses a narrow form-factor to make it suitable to fit into narrow T8 enclosures.

To minimize EMI, current loops of the gate drive, snubber circuit, output diode and main MOSFET switching loop should be kept as small as possible. Ground of the IC, sense resistor, aux winding and Y-capacitor should all go to one central ground point on the input capacitor ground. Capacitors on the IC COMP pin, ZCD pin and MULT pin should be as close as possible to the IC.



Top silk (Component location)



Top trace



Bottom trace



Figure 6. PCB Layout

## 8. Summary

With the help of this step by step design guide and the [RT7302 design tool](#), the user is able to quickly design a LED driver that fulfills the requirements for high performance offline LED drivers. The absence of secondary side sensing greatly simplifies the mechanical design, and allows small form-factor PCB design.

When all guidelines are followed, the design should fulfill EMI and pass the surge tests. Although this reference design is for an 18W LED driver, [RT7302](#) can be used in a wide range of LED driver designs, ranging from 8W ~ 60W.

### Related Parts

<a href="#">RT7302</a>	Primary-Side-Regulation Dimmable LED Driver Controller with Active PFC	 <a href="#">Datasheet</a>
<a href="#">RT7304</a>	Primary-Side-Regulation Dimmable LED Driver Controller with Active PFC	 <a href="#">Datasheet</a>

### Next Steps

Richtek Newsletter	<a href="#">Subscribe Richtek Newsletter</a>
Download	<a href="#">Download PDF</a>
Application	<a href="#">LED Lighting</a>

## Richtek Technology Corporation

14F, No. 8, Tai Yuen 1<sup>st</sup> Street, Chupei City  
Hsinchu, Taiwan, R.O.C.  
Tel: 886-3-5526789

Richtek products are sold by description only. Richtek reserves the right to change the circuitry and/or specifications without notice at any time. Customers should obtain the latest relevant information and data sheets before placing orders and should verify that such information is current and complete. Richtek cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in a Richtek product. Information furnished by Richtek is believed to be accurate and reliable. However, no responsibility is assumed by Richtek or its subsidiaries for its use; nor for any infringements of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of Richtek or its subsidiaries.