

RT1985/RT1986/RT1987/RT1988 Ideal Diode Protection Switch: Design Considerations and Applications

Shihchun Liu | AN089

March 2026



In modern electronic systems, efficient power management is crucial to ensuring reliable operation and extending battery life. Protection switches have become essential components in simplifying power control and protection for various loads. Compared to discrete MOSFET solutions, integrated protection switches offer benefits such as smaller size, enhanced protection features, and simplified design processes.

The [RT1985/RT1986/RT1987/RT1988](#) family is the high-performance Ideal Diode Protection Switch, specifically designed to enhance the power management of modern electronic systems such as USB-C/Thunderbolt power delivery, docking stations, and Power ORing configurations. This application note provides a detailed overview of the product's features, applications, and key design considerations.

Table of Contents

1	Key Features of Protection Switches	3
1.1	Power Control (On/Off Switching).....	3
1.2	Programmable Soft-Start and Inrush Current Control	4
1.3	Start-Up Short-Circuit Protection (SCP).....	5
1.4	Reverse Current Blocking	6
1.5	Overvoltage Protection (OVP)	7
1.6	Over-Temperature Protection.....	8
1.7	Low On-Resistance (20mΩ).....	9
1.8	Ultra-Low Quiescent Current	9
2	Application Examples	9
2.1	USB-C/Thunderbolt Power Delivery	9
2.2	Docking Stations	10
2.3	Power ORing Applications	10
3	Conclusion	11

1 Key Features of Protection Switches

Featuring low forward voltage, programmable soft-start, start-up short-circuit protection, and robust fault protection mechanisms, the [RT1985/RT1986/RT1987/RT1988](#) family simplifies power path management while increasing system reliability. Compared to discrete MOSFET implementations, this family offers a smaller footprint, easier design integration, and superior protection features.

Product	Operation Vin	Maximum Continuous Current	OVP Threshold	Package
RT1985	3.4V to 23V	8A	Fixed	VDFN-12TL 3x3
RT1986	3.4V to 23V	5.5A	Fixed	VDFN-12TL 3x3
RT1987	3.4V to 32V	8A	Programmable	VDFN-12T1L 3x3
RT1988	3.4V to 53V	8A	Programmable	VDFN-20TL 5.2x4

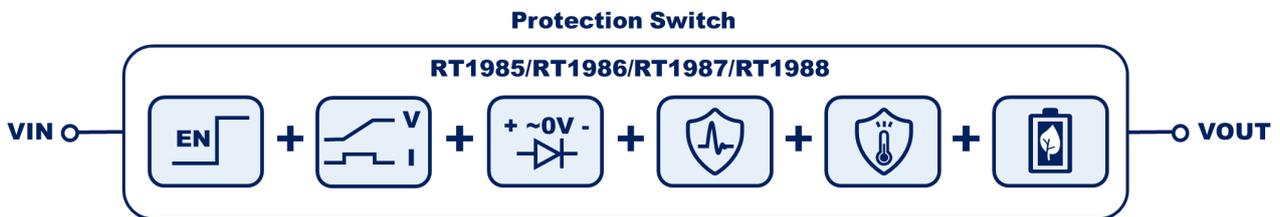


Figure 1. Protection Switch Features

1.1 Power Control (On/Off Switching)

Protection switches provide a straightforward method to control the connection and disconnection of power to specific loads without mechanical relays. This allows for better power sequencing and dynamic power management. The [RT1985](#), [RT1986](#), [RT1987](#), or [RT1988](#) provides precise power path control through an active-high EN pin. When EN is asserted high and the input voltage exceeds the UVLO threshold, the power path is enabled with a defined delay and controlled ramp-up behavior.

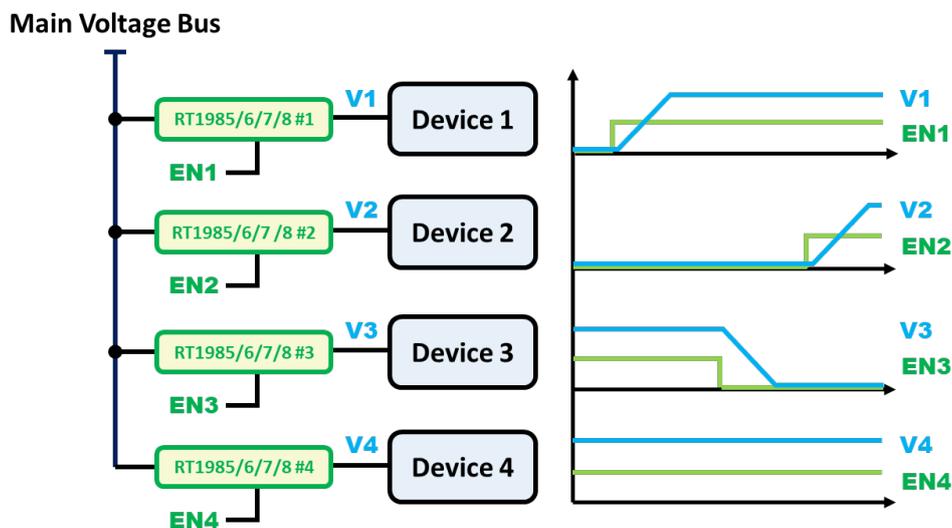


Figure 2. Enable Control of the Protection Switch

1.2 Programmable Soft-Start and Inrush Current Control

Many protection switches incorporate built-in soft-start features by controlling the gate drive voltage, allowing a gradual increase in output voltage and current. The [RT1985](#), [RT1986](#), [RT1987](#), or [RT1988](#) includes an adjustable soft-start feature. By adjusting an external soft-start capacitor, designers can set the VOUT slew rate and limit the inrush current. This prevents voltage glitches on the main bus, protecting sensitive devices that share the same supply. This feature is critical for systems with large capacitance. Refer to the datasheet for detailed soft-start capacitor design guidelines.

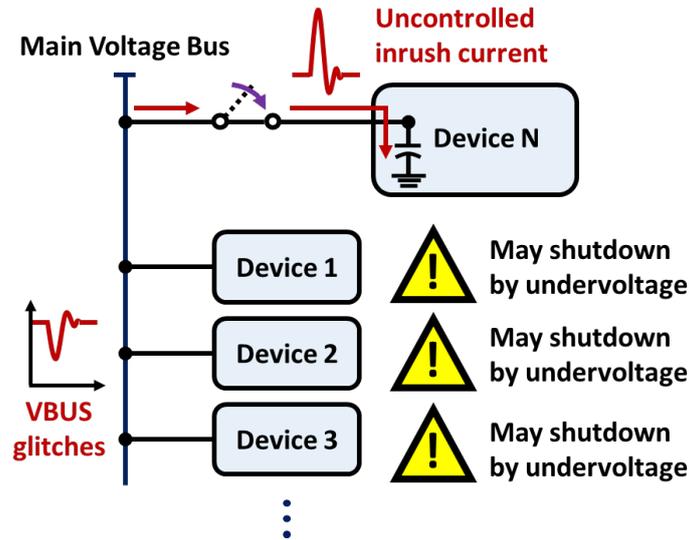


Figure 3. Startup without the Inrush Current Control

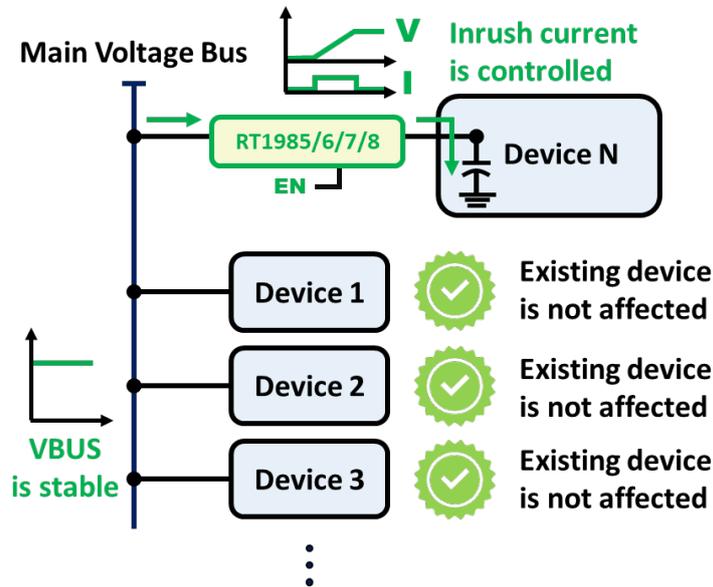


Figure 4. Startup with the Inrush Current Control



Figure 5. [RT1985](#) Soft-Start Test Results

1.3 Start-Up Short-Circuit Protection (SCP)

During startup, the [RT1985](#), [RT1986](#), [RT1987](#), or [RT1988](#) monitors the output current. If an excessive inrush current or a hard short is detected, the device safely shuts down and retries after a defined delay, ensuring robust protection even under fault conditions.

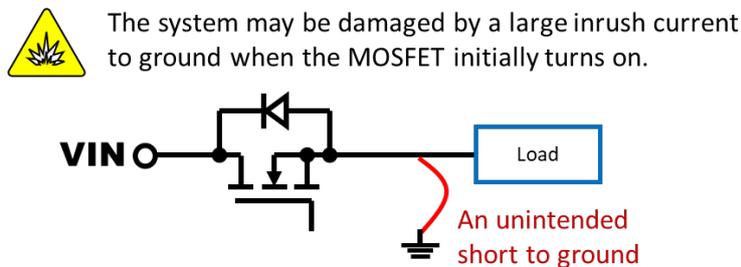


Figure 6. A MOSFET is used as a protection switch

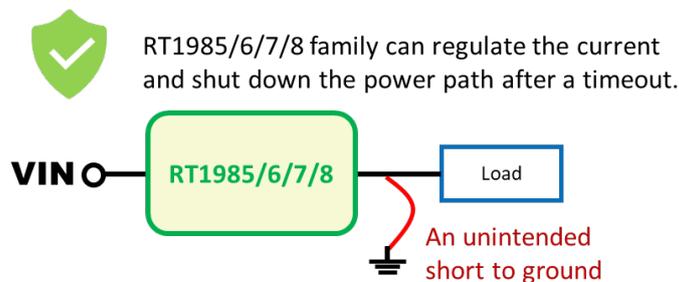


Figure 7. The [RT1985/RT1986/RT1987/RT1988](#) is used as a protection switch

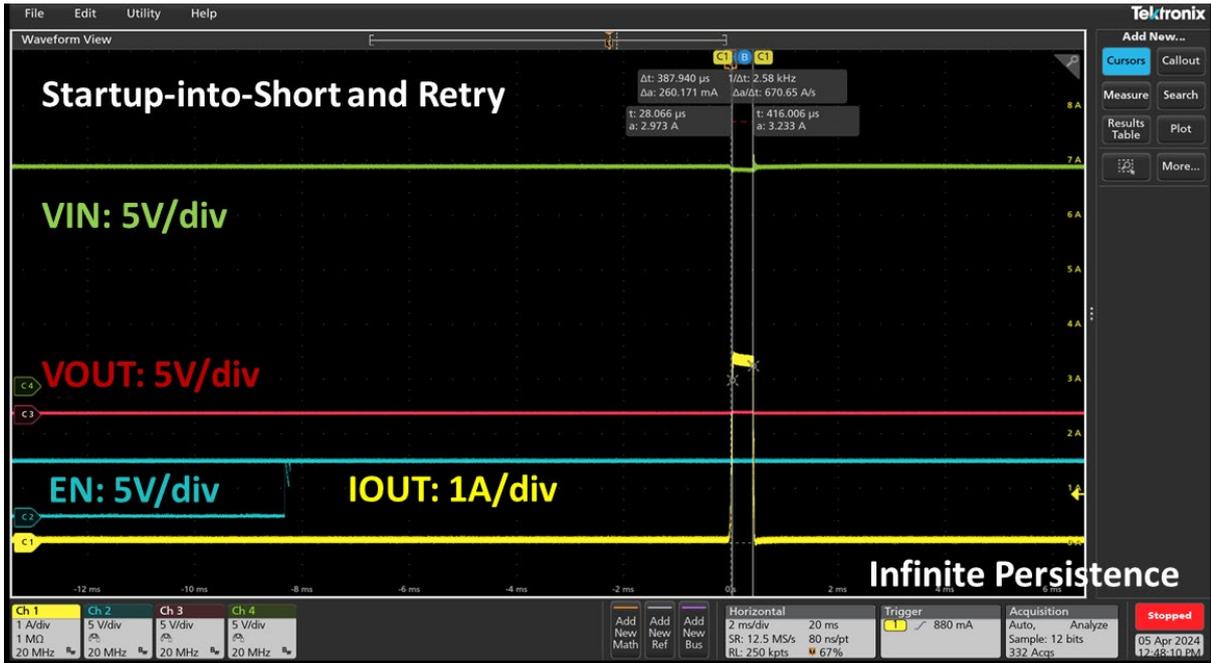


Figure 8. [RT1985](#) Startup-into-Short and Retry Test Results

1.4 Reverse Current Blocking

Some protection switches offer reverse current blocking to prevent current from flowing backward from the output to the input, which is especially important in redundant power source systems. The [RT1985](#), [RT1986](#), [RT1987](#), or [RT1988](#) offers Ideal Diode True Reverse Current Blocking (TRCB) capability, regulating the forward voltage drop and preventing reverse current flow from VOUT to VIN. This is essential in ORing applications where multiple power sources share a common load.

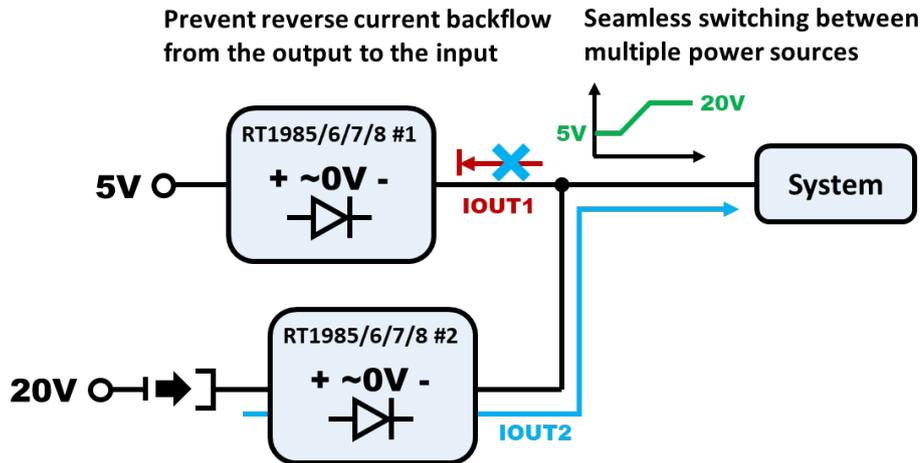


Figure 9. Reverse Blocking from the Output to the Input



Figure 10. [RT1985](#) Reverse Blocking Protection Test Results

1.5 Overvoltage Protection (OVP)

Some protection switches integrate overvoltage protection to safeguard downstream circuitry from input voltage spikes or abnormal conditions. The [RT1985](#), [RT1986](#), [RT1987](#), or [RT1988](#) includes OVP functionality that disconnects the load when the input voltage exceeds a defined threshold, preventing damage to sensitive components. This feature is particularly valuable in USB-C and power ORing systems, where unpredictable input sources may expose the system to voltage surges.

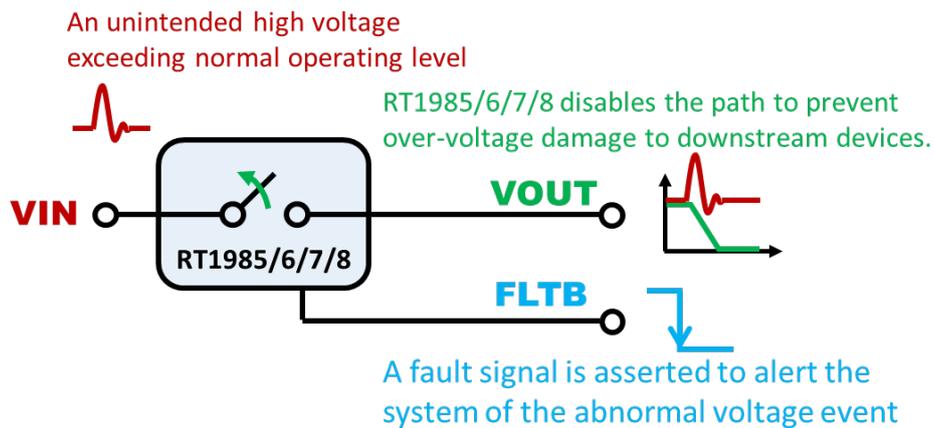


Figure 11. Overvoltage Protection from Excessive Input Voltage



Figure 12. RT1985 Overvoltage Protection Test Results

1.6 Over-Temperature Protection (OTP)

Advanced protection switches integrate thermal protection mechanisms. If the device's junction temperature exceeds a critical threshold, it automatically turns off to prevent permanent damage. The RT1985, RT1986, RT1987, or RT1988 actively monitors the die temperature. If an excessive temperature (~140°C) is detected, the device disconnects the load and asserts a fault indication, enhancing system safety.

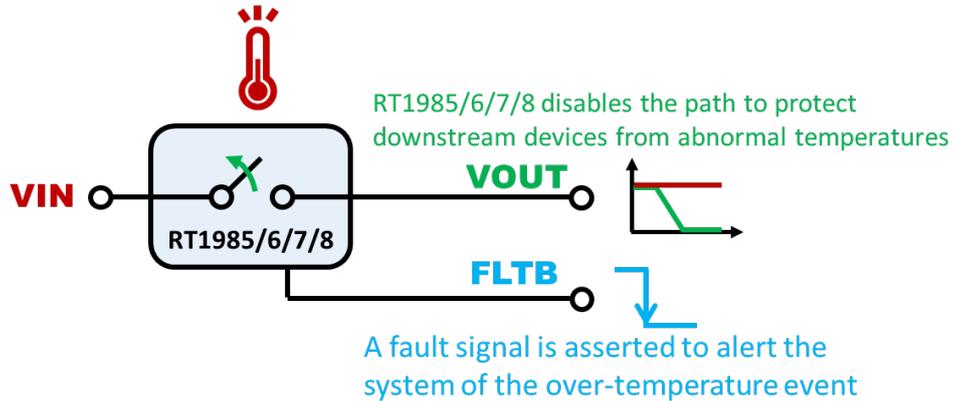


Figure 13. Over-Temperature Protection from Abnormal Thermal Conditions

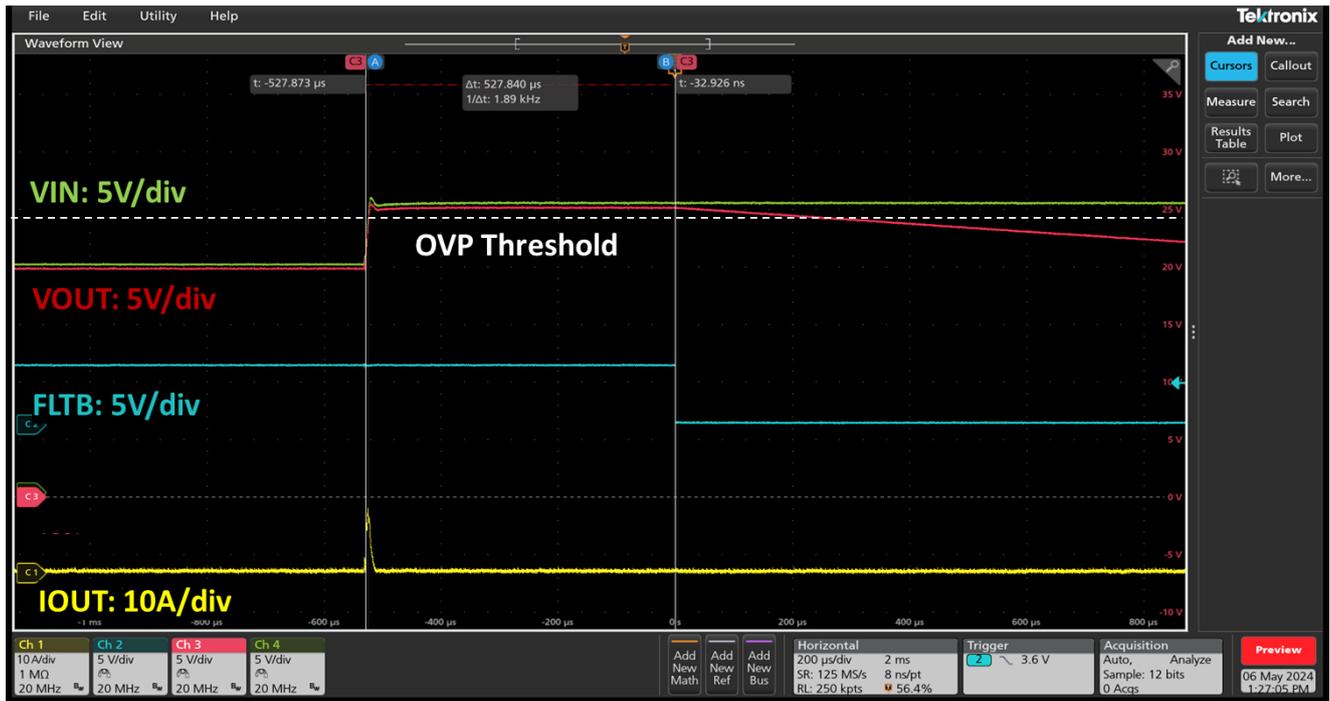


Figure 14. [RT1985](#) Over-Temperature Protection Test Results

1.7 Low On-Resistance (20mΩ)

The [RT1985](#), [RT1986](#), [RT1987](#), or [RT1988](#) adopts advanced process technology to reduce the on-resistance (RON) of the internal MOSFET to as low as 20mΩ, effectively minimizing power loss during high current transmission ($P = I^2R$). This not only reduces device heating but also improves overall thermal efficiency.

1.8 Ultra-Low Quiescent Current

The [RT1985](#), [RT1986](#), [RT1987](#), or [RT1988](#) features an ultra-low quiescent current design, meaning that the IC itself consumes minimal power under no-load or light-load conditions. This further optimizes overall system power consumption and extends battery life, making it well-suited for portable devices such as laptops and tablets.

2 Application Examples

2.1 USB-C/Thunderbolt Power Delivery

Protection switches are critical in USB-C and Thunderbolt applications, where they control and protect power delivery to devices. They ensure safe connection and disconnection during dynamic power negotiation processes, managing inrush currents, and preventing backflow. [Figure 15](#) illustrates the [RT1985](#) used for sink and source control in a dual-port USB PD application.

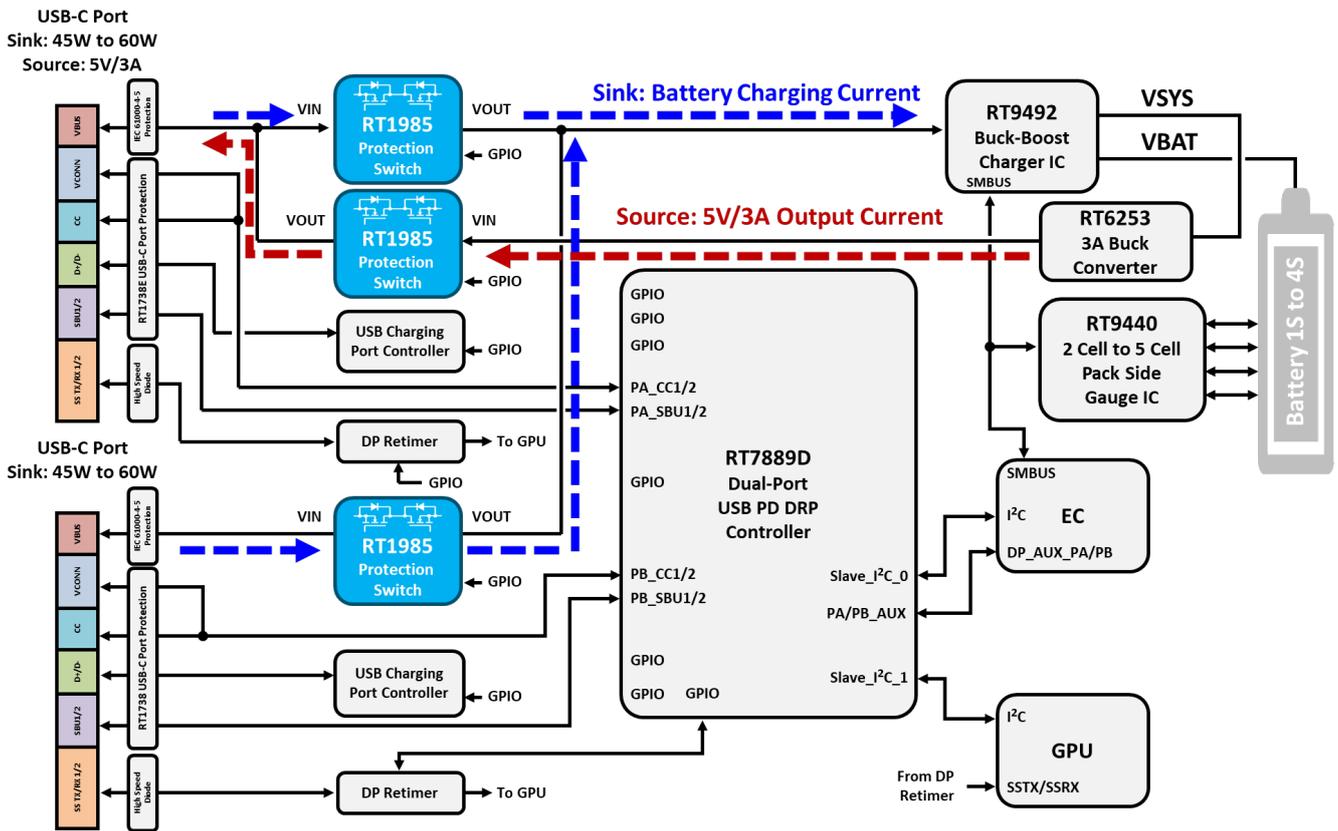


Figure 15. RT1985 for Sink and Source Control in a Dual-Port USB PD Application

Note 1. The above system diagram is for reference only. Actual products should be evaluated and adjusted based on your specific application requirements. For further assistance, please contact our regional office.

2.2 Docking Stations

In docking stations for laptops and tablets, protection switches are used to selectively enable or disable power to various ports and peripherals, helping optimize overall system efficiency, minimize standby power losses, and provide fault isolation.

2.3 Power ORing Applications

Protection switches with true reverse current blocking capability enable reliable power ORing. This allows seamless switching between multiple power sources (such as adapters, batteries, or auxiliary supplies) without backfeeding, ensuring system continuity and reliability.

3 Conclusion

Proper integration of protection switches enhances system reliability, reduces design complexity, and optimizes energy efficiency. As systems become increasingly complex, protection switches will continue to play a vital role in intelligent power distribution strategies. The [RT1985](#), [RT1986](#), [RT1987](#), or [RT1988](#) offers a highly integrated and robust solution for power path control, featuring Ideal Diode reverse current blocking, programmable soft-start, and advanced fault protection. Its compact design and versatile protection features make it ideal for demanding applications such as USB-C sink power delivery, docking stations, and power ORing systems. Leveraging the [RT1985](#), [RT1986](#), [RT1987](#), or [RT1988](#) simplifies power management design, increases system reliability, and enhances the end-user experience in next-generation electronic products.

To stay informed with more information about our products, please [subscribe to our newsletter](#).

Richtek Technology Corporation

14F, No. 8, Taiyuan 1st St., Zhubei City,
Hsinchu County 302082, Taiwan (R.O.C.)
Tel: 886-3-5526-789

Richtek products are sold by description only. Richtek reserves the right to change the circuitry and/or specifications without notice at any time. Customers should obtain the latest relevant information and data sheets before placing orders and should verify that such information is current and complete. Richtek cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in a Richtek product. Information furnished by Richtek is believed to be accurate and reliable. However, no responsibility is assumed by Richtek or its subsidiaries for its use; nor for any infringements of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of Richtek or its subsidiaries.

Copyright © 2026 Richtek Technology Corporation. All rights reserved. **RICHTEK** is a registered trademark of Richtek Technology Corporation.